

California State University, Northridge
College of Engineering & Computer Science
Electrical and Computer Engineering
Department

ECE 443L Digital Electronics Laboratory
Report 10

CMOS based Comparator Circuit Design,
Simulation and Experimental Test as well as
Analysis

By Evan Thomas, Haroutun Haroutunian,
Clayton Lawton



Professor: Sequare Daniel-Berhe

Abstract:

Lab 4 exposes students of Comparators and their functionalities in everyday electronics. A comparator is simply a device which compares 2 input voltages or currents and outputs indicating which signal was larger. Comparators are largely utilized in Analog-to-digital converters, which are found in almost every advanced electronic.

Key Terms:

Comparator, ADC, converter

Simulation and Experimental Result:


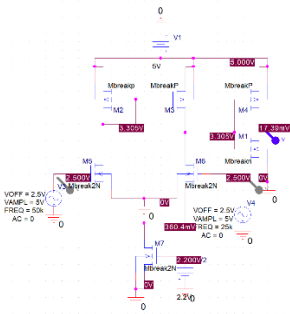


Figure 4.1: Case 1 EVAN Comparator Schematic @ 25kHz and 50kHz

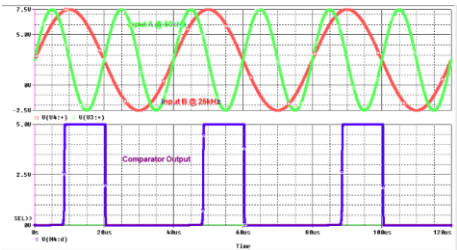

Trace Color	Trace Name	X Values	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	Max Y	Min Y	Avg Y
CURSOR 12	V(M4-d)	0.000 17.385m 17.385m	0.000 0.000	0.000 0.000	17.385m	17.385m	17.385m
	V(V4-+)	2.5000 2.5000	0.000 2.4826	2.5000 2.5000	2.5000	2.5000	2.5000
	V(V3-+)	2.5000 2.5000	0.000 2.4826	2.5000 2.4826	2.5000	2.5000	2.5000

Figure 4.2: Case 1 EVAN Comparator Waveform and Cursor @ 25kHz and 50kHz

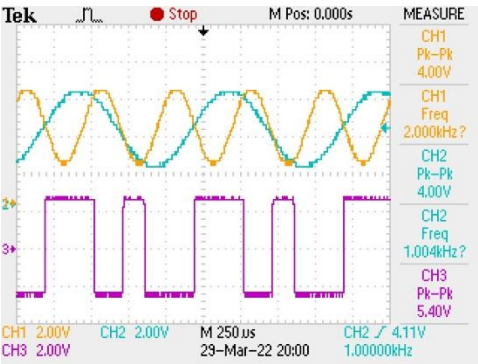


Figure 4.3: Case 1 EVAN Comparator Circuit Result @ 1kHz and 2kHz

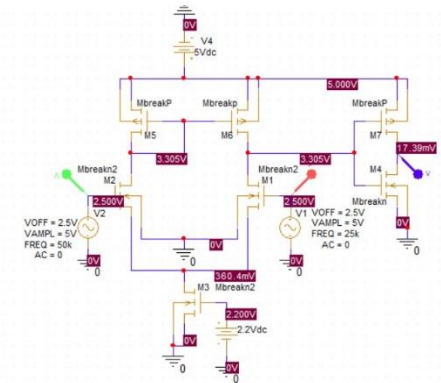


Figure 4.4: Case 1 CLAYTON Comparator Schematic @ 25kHz and 50kHz

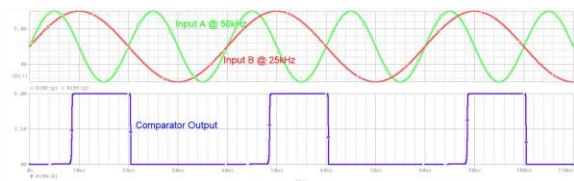


Figure 4.5: Case 1 CLAYTON Comparator Waveform @ 25kHz and 50kHz


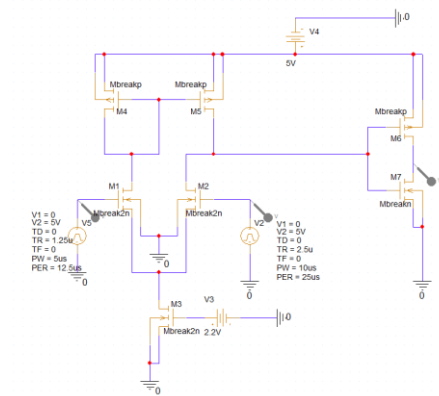


Figure 4.6: Case 2 HAROUTUN Comparator Schematic @ 20kHz and 40kHz

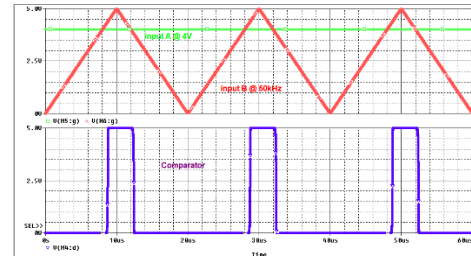

Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	0.000			
	X Values	0.000	0.000	0.000	Y1 - Y1(Cursor1)	Y2 - Y2(Cursor2)	Max Y	Min Y	Avg Y
CURSOR 1 X	V(M4.d)	21.662n	21.662n	0.000	0.000	0.000	21.662n	21.662n	21.662n
	V(M5.g)	4.0000	4.0000	0.000	4.0000	4.0000	4.0000	4.0000	4.0000
	V(M6.g)	5.0000u	5.0000u	0.000	4.9783u	4.9783u	5.0000u	5.0000u	5.0000u

Figure 4.9: Case 3 EVAN Comparator Waveform @ 50kHz and 4V

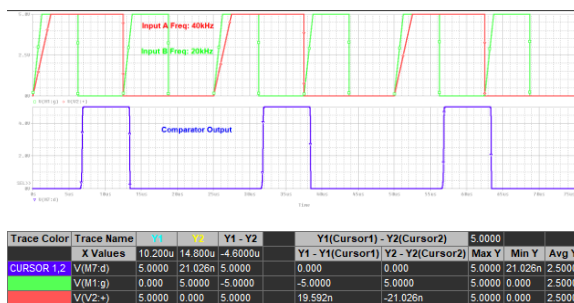


Figure 4.7: Case 2 HAROUTUN Comparator Waveform @ 20kHz and 40kHz

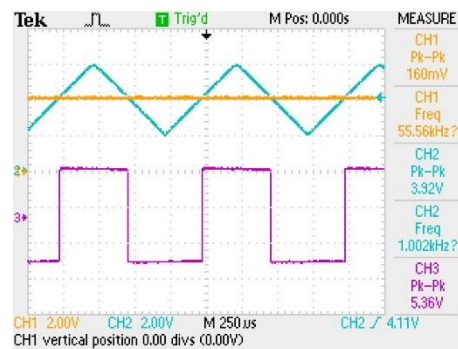


Figure 4.10: Case 3 EVAN Comparator Circuit Output @ 1kHz and 3.92V

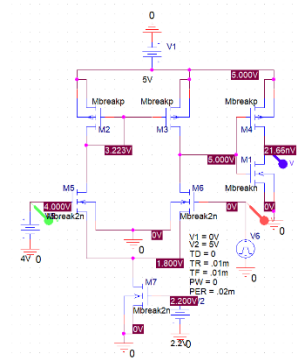


Figure 4.8: Case 3 EVAN Comparator Schematic @ 50kHz and 4V

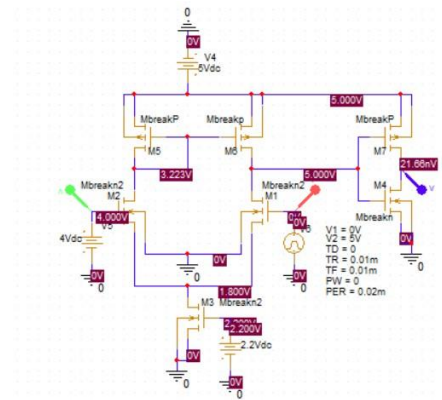


Figure 4.11: Case 3 CLAYTON Comparator Schematic @ 50kHz and 4V

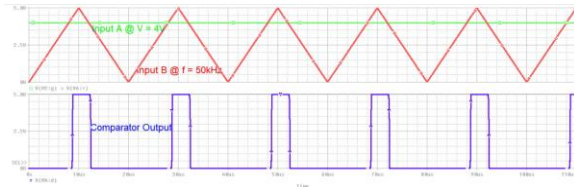


Figure 4.12: Case 3 CLAYTON Comparator Waveform @ 50kHz and 4V

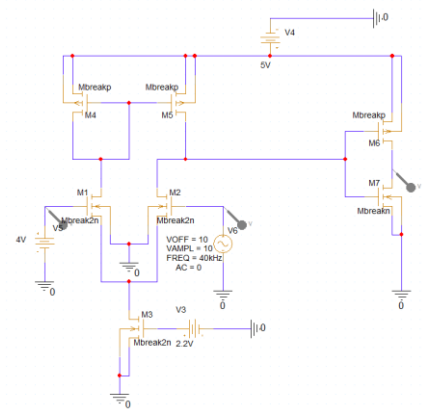


Figure 4.13: Case 4 HAROUTUN Comparator Schematic @ 40kHz and 4V

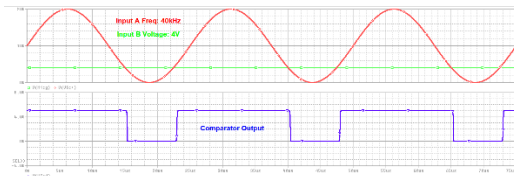


Figure 4.14: Case 4 HAROUTUN Comparator Waveform @ 40kHz and 4V

Trace Color	Trace Name	V1	V2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	15.997	
	X Values	31.351u	31.351u	0.000	Y1 - Y1(Cursor1)	Y2 - Y2(Cursor2)	Max Y Min Y Avg Y
	V(M7-d)	5.000u	5.000u	0.000	-14.997	1.0000	5.0000 5.0000 5.0000
CURSOR 2	V(M1-g)	4.000u	4.000u	0.000	-15.997	0.000	4.0000 4.0000 4.0000
CURSOR 1	V(V6-v)	19.997	19.997	0.000	0.000	15.997	19.997 19.997 19.997


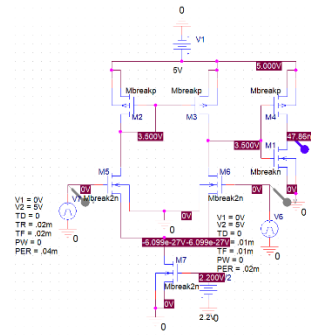


Figure 4.15: Case 5 EVAN Comparator Waveform @ 25kHz and 50kHz

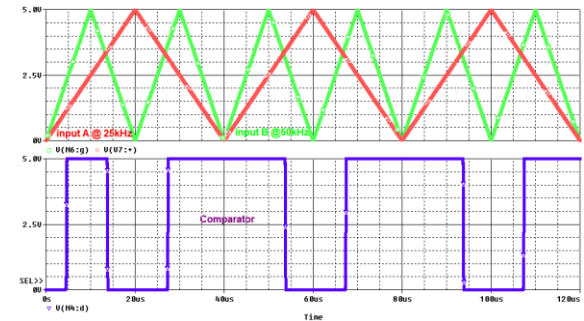

Trace Color	Trace Name	V1	V2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	0.000	
	X Values	0.000	0.000	0.000	Y1 - Y1(Cursor1)	Y2 - Y2(Cursor2)	Max Y Min Y Avg Y
CURSOR 1	V(M4-d)	47.858u	47.858u	0.000	0.000	47.858u	47.858u 47.858u 47.858u
	V(M6-g)	5.0000u	5.0000u	0.000	4.9521u	4.9521u	5.0000u 5.0000u 5.0000u
	V(V7-v)	2.5000u	2.5000u	0.000	2.4521u	2.4521u	2.5000u 2.5000u 2.5000u

Figure 4.16: Case 5 EVAN Comparator Waveform @ 25kHz and 50kHz

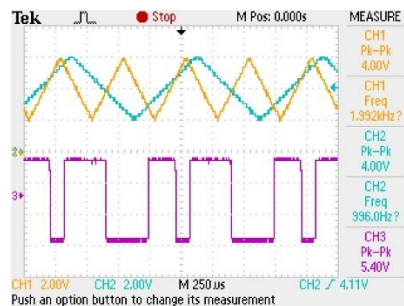


Figure 4.17: Case 5 EVAN Comparator Circuit Output @ 2kHz and 996Hz

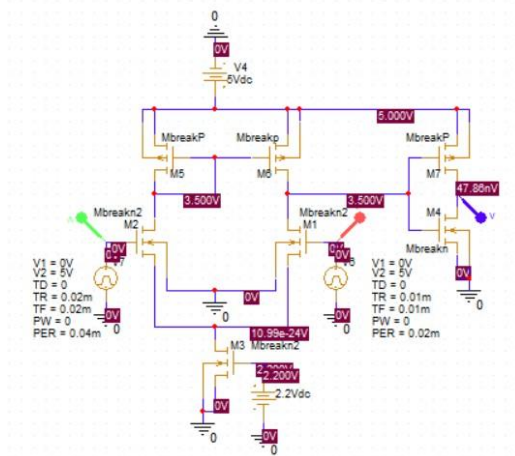


Figure 4.18: Case 5 CLAYTON Comparator Schematic @ 25kHz and 50kHz

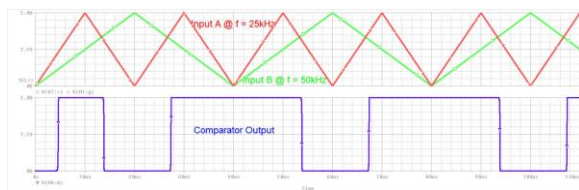


Figure 4.19: Case 5 CLAYTON Comparator Waveform @ 25kHz and 50kHz


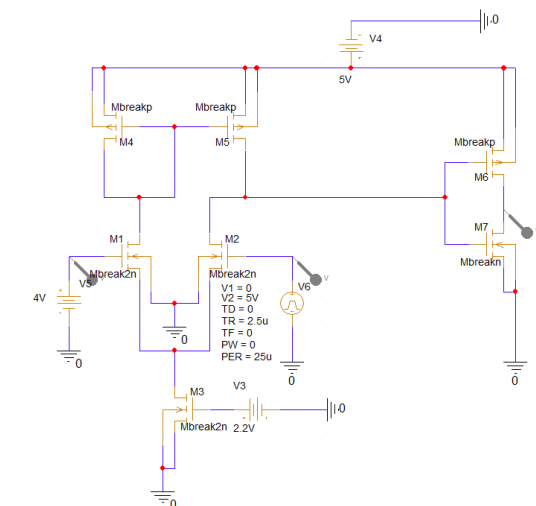


Figure 4.20: Case 6 HAROUTUN Comparator Schematic @ 40kHz and 4V

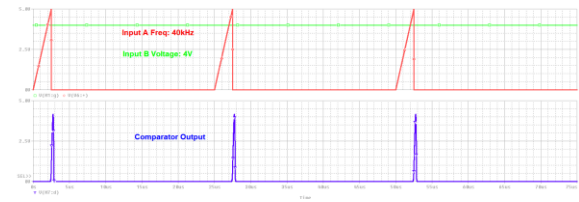

Trace Color	Trace Name	X Values	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	1.0000	Max Y	Min Y	Avg Y
	V(M7.d)	817.545m 23.163n 817.545m	-4.1825	-4.0000	817.545m 23.163n 488.772m			
	CURSOR 2 V(M1.g)	4.0000 4.0000 0.000	-1.0000	0.000	4.0000 4.0000 4.0000			
	CURSOR 1 V(V6.+)	5.0000 0.000 5.0000	0.000	-4.0000	5.0000 0.000 2.5000			

Figure 4.21: Case 6 HAROUTUN Comparator Waveform @ 40kHz and 4V

Conclusion:

Students not only constructed a comparator on the advanced software PSpice but recreated the circuit on a breadboard. As seen in figure 4.17, the comparator functions properly, indicating which input signal was higher. Comparators are found in almost every electronics which allows engineers to produce circuits based upon the comparative result of 2 signals.